

function
generator



T-conn.



Ch. 1



Breadboard



Ch. 2



note: connect to Ch. 2 across the capacitor
for a low pass filter and across the resistor
for a high pass filter